

CHAPTER

6

# **Modeling Combinational Logic Circuits**

## Chapter 6 Contents

|  |            |
|--|------------|
| <b>Modeling Combinational Logic .....</b>                        | <b>133</b> |
| <b>Logical/Arithmetic Equations .....</b>                        | <b>134</b> |
| Example 6.1 Equations modeled using continuous assignments ..... | 134        |
| <b>Logical Structure Control .....</b>                           | <b>135</b> |
| Example 6.2 Parentheses used to control logical structure .....  | 135        |
| <b>Multiplexers .....</b>  | <b>136</b> |
| Example 6.3 One-bit wide 2-1 multiplexer .....                   | 136        |
| Example 6.4 Modeling styles of a 4-1 multiplexer .....           | 137        |
| Example 6.5 Two-bit wide 8-1 multiplexer using <b>case</b> ..... | 139        |
| <b>Encoders .....</b>  | <b>141</b> |
| Example 6.6 An 8-3 binary encoder .....                          | 141        |
| <b>Priority Encoders .....</b>                                   | <b>145</b> |
| Example 6.7 An 8-3 binary priority encoder .....                 | 145        |
| <b>Decoders .....</b>  | <b>148</b> |
| Example 6.8 A 3-8 binary decoder .....                           | 148        |
| Example 6.9 A 3-6 binary decoder with enable .....               | 150        |
| Example 6.10 Four bit address decoder .....                      | 152        |
| Example 6.11 Generic N to M bit binary decoder .....             | 154        |
| <b>Comparators .....</b>   | <b>157</b> |
| Example 6.12 Simple comparator .....                             | 157        |
| Example 6.13 Multiple comparison comparator .....                | 158        |
| <b>ALU .....</b>   | <b>159</b> |
| Example 6.14 An arithmetic logic unit .....                      | 159        |

## Modeling Combinational Logic

This chapter demonstrates the different ways in which purely combinational logic may be modeled. It does not include tri-state logic which is covered separately in Chapter 10. The types of combinational logic circuit commonly used in digital design and covered in this chapter are listed in Table 6.1.

|                              |
|------------------------------|
| logical/arithmetic equations |
| logical structure control    |
| multiplexers                 |
| encoders                     |
| priority encoders            |
| decoders                     |
| comparators                  |
| ALUs                         |

**Table 6.1 Functional types of combinational logic circuit**

These more standard functional types of circuit are used in both control path and datapath structures. Typically each circuit type can be modeled in different ways using **if**, **case**, and **for** statements etc. Additionally for VHDL only, the concurrent selected and conditional signal assignments can also be used. The selected signal assignment is synonymous with the **if** statement and the conditional signal assignment is synonymous with the **case** statement, but reside outside a **process**. This means they are always active and so may increase the time it takes to simulate a model when compared to using a **process** with a sensitivity list. Also, the VHDL **for-loop** may include one or more **next** or **exit** statements. The **next** statement causes a jump to the next loop iteration, while the **exit** statement causes an exit from the **for-loop** altogether. There is no equivalent to the **next** or **exit** statements in Verilog. The VHDL **while-loop** statement, and the Verilog **forever** and **while-loop** statements, are not often used to model combinational logic; their loop range must have a static value at synthesis compile time so that a predetermined amount of logic can be synthesized. They are not supported by the synthesis tools from VeriBest Incorporated.

Note, that when modeling combinational logic, the sensitivity list of a **process** statement (VHDL) or the event list of an **always** statement (Verilog), must contain all inputs used in the particular statement. If it does not, the model will still synthesize correctly, but may not simulate correctly. This is because **process/always** statements are concurrent and will not be triggered into being executed when the omitted signals change, and means the output signals will not be updated.

Because the examples in this chapter are relatively small for demonstration purposes, VHDL models use mostly signal assignments and relatively few variable assignments. VHDL models with more code in a **process**, typically use more variable assignments. Variables and constants are used in the computation of signal values, see Chapter 4. A number of VHDL model versions in this chapter use **for-loop** statements. It is better to use only variable assignments, and not signal assignments in **for-loop** statements. This is not mandatory as identical circuits will be synthesized, but it will simulate faster for reasons given in Chapter 4.

The logic synthesized from the majority of the models in this chapter have little or no inherent logical structure. This means area, timing and power characteristics are often considerably improved when the synthesized circuit is optimized. Logic optimization breaks down the logical structure of a circuit and creates a new one in the process of attempting to improve any area, timing or power requirements that have been specified.

The following sections describe each of the circuit functions listed in Table 6.1. Shifters, multipliers and dividers can also be modeled using synchronous logic and are included in Chapter 9.

## Logical/Arithmetic Equations


Both logical and arithmetic equations may be modeled using the logical and arithmetic operators in the expressions of continuous data flow assignments, see Example 6.1.

### Example 6.1 Equations modeled using continuous assignments

Logical and arithmetic equations are modeled using continuous data flow assignments, incorporating both logical and arithmetic operators. Both concurrent (outside **process/always**) and sequential (inside **process/always**) assignments are shown.

VHDL signals S1 and S2 and variables V1 and V2, have identical names in the Verilog model for comparison, but are all variables of type **reg** in the Verilog model. The Verilog variables V1 and V2 are not local to the sequential block as the variables are in the VHDL model. Although Verilog supports locally defined data types of type **reg**, this is not generally supported by synthesis tools. The VHDL output Y1 is defined from a concurrent continuous assignment and so the Verilog equivalent must be of type **wire**. The data type of Y1 could have been explicitly defined as a **wire**, for example, "**wire** Y1;", however, this is not necessary as type **wire** is implied by default as defined by the Verilog language.
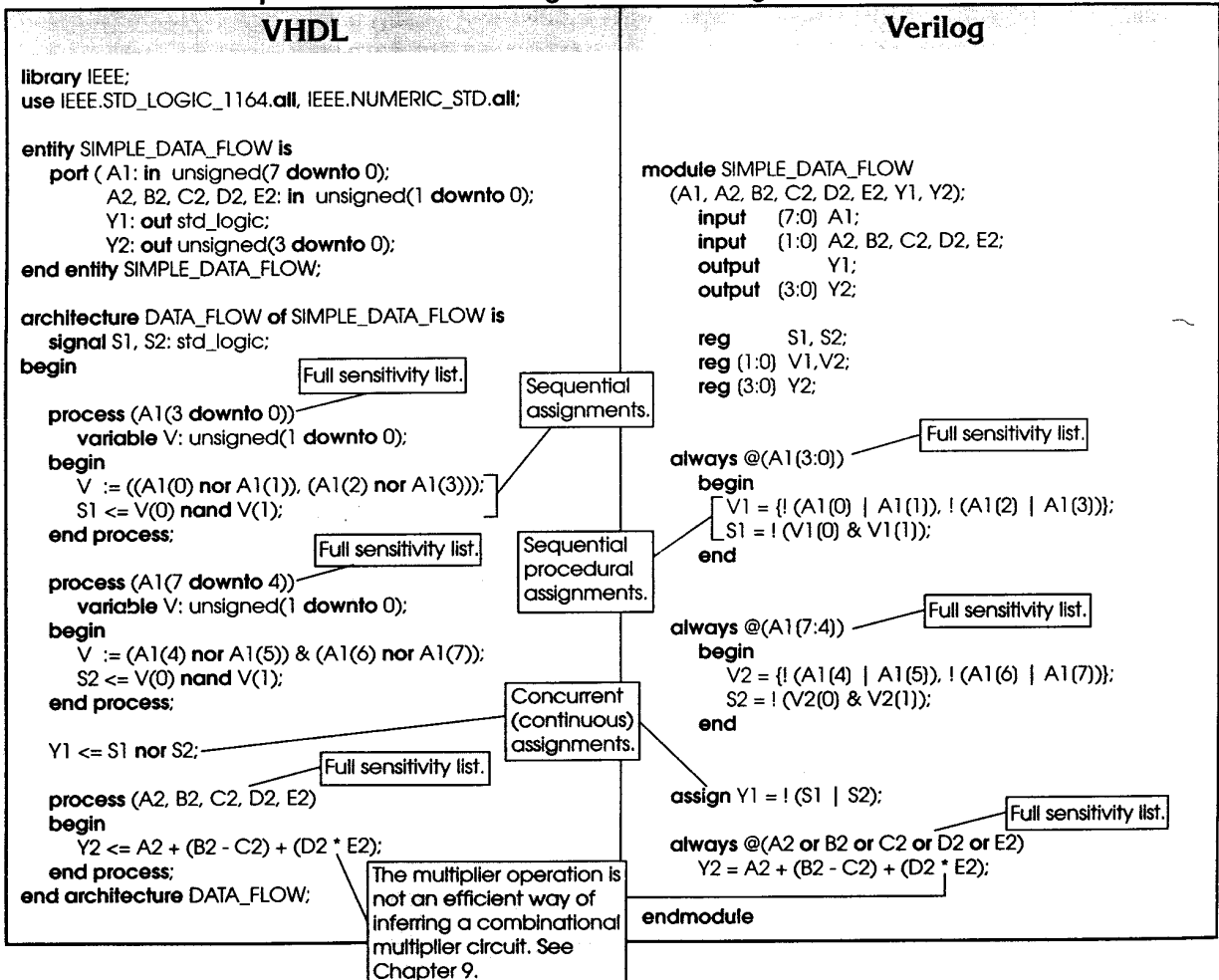
#### Mathematical equations modeled using continuous assignments




## Logical Structure Control

Parentheses can be used for coarse grain control of synthesized logic structure. Logic optimization can still be used to break down all, or most, of a circuit's logic structure and restructure it in the process of attempting to meet specific constraints. However, the use of parentheses in the model's expressions can make the optimizer's job far easier and less cpu intensive, but more importantly, the optimizer may not be able to achieve such good results that careful choice of parentheses can bring, see Example 6.2.

### Example 6.2 Parentheses used to control logical structure

Parentheses are used to control the structure of inferred adders. The model contains two assignments, each implying the synthesis of three adders. The first assignment to Y1 does not use parentheses and so defaults to a left to right priority; this results in a worst case timing delay which passes through three adders. The second assignment to Y2 does use parentheses for a more coarse grain structural control and infers a circuit structure whose longest timing delay this time passes through only two adders instead of three.
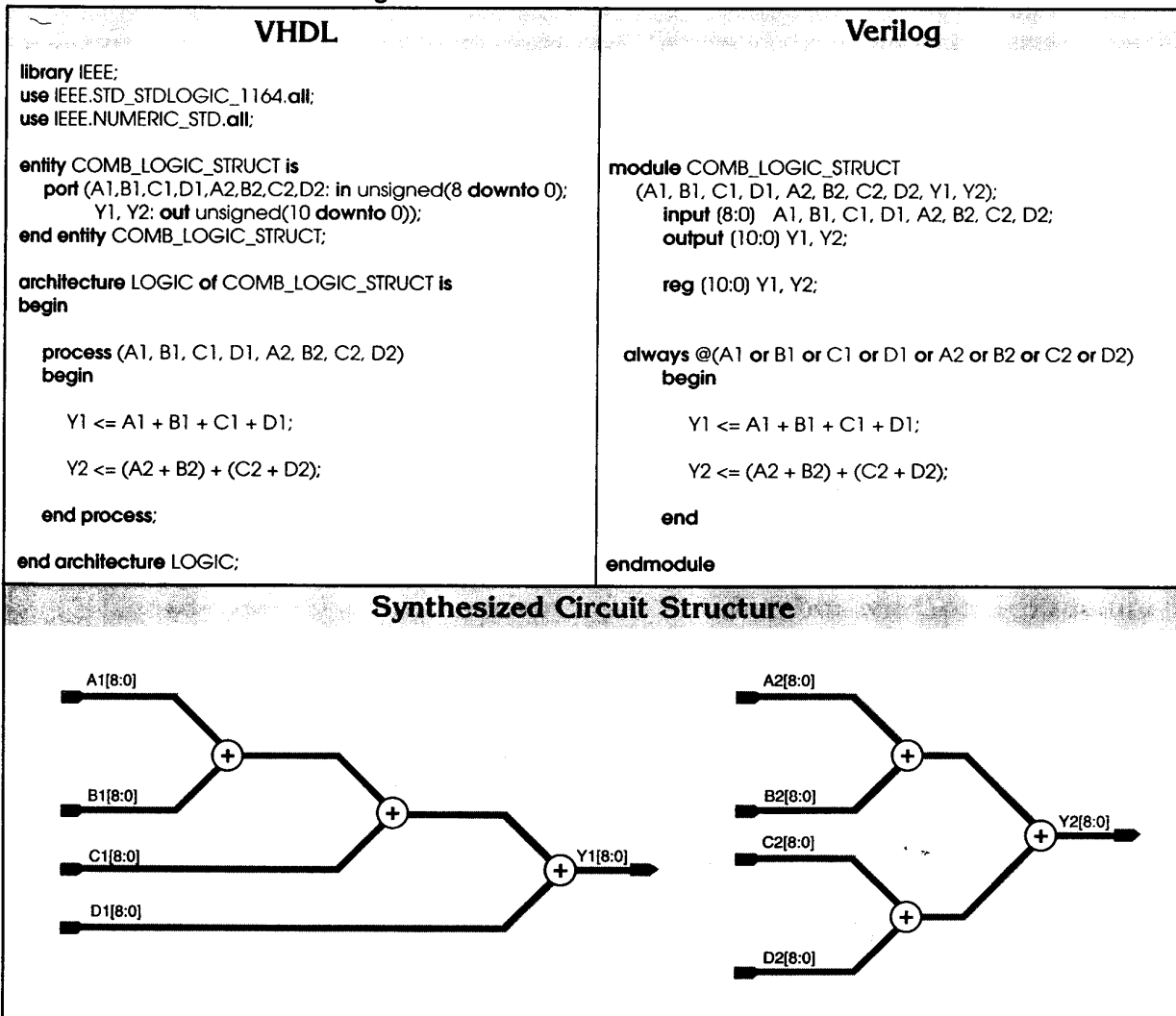
#### Parentheses used to control logical structure



## Multiplexers

A multiplexer selectively passes the value of one, of two or more input signals, to the output. One or more control signals control which input signal's value is passed to the output, see Figure 6.1. Each input signal, and the output signal, may represent single bit or multiple bit busses. The select inputs are normally binary encoded such that  $n$  select inputs can select from one of up to  $2^n$  inputs.

 



Figure 6.1 The Multiplexer

RTL level synthesis tools are not particularly good at identifying multiplexer type functions and mapping them directly onto multiplexer macro cells in a given technology library. If this is desired a multiplexer macro cell should be explicitly instantiated in the HDL model. However, a multiplexer circuit is often better implemented in cell primitives as they can be optimized with their surrounding logic and often produce a more optimal overall circuit implementation. Example 6.3 shows three ways of modeling a 2-1 multiplexer. Example 6.4 shows a 4-1 multiplexer modeled in several different ways and Example 6.5 shows a 2-bit wide 8-1 multiplexer.

### Example 6.3 One-bit wide 2-1 multiplexer

The model of the one-bit wide 2-1 multiplexer described above is shown modeled using the `if` statement in its most simplest form. Multiplexer output `Y1` is derived concurrently via a selected signal assignment in VHDL and a conditional continuous assignment in Verilog. The second and third multiplexer outputs, `Y2` and `Y3`, are derived from an `if` statement. The first `if` statement defines a default output value for `Y2` in an assignment immediately before the `if` statement, while the second `if` statement uses the more normal method of using an `else` clause.

#### One bit wide 2-1 multiplexer

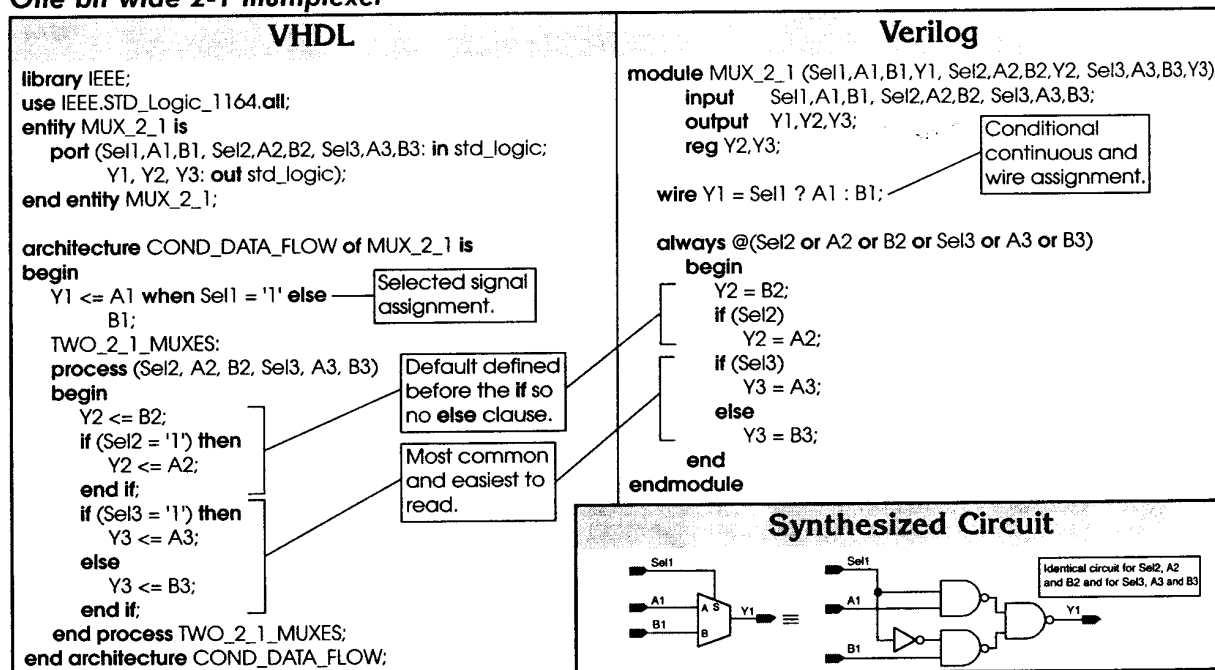


**Example 6.4 Modeling styles of a 4-1 multiplexer**

Five ways of modeling a 4-1 multiplexer in VHDL, and three ways of modeling it in Verilog are indicated. They are:


1. one **if** statement with multiple **elsif/else if** clauses,
2. a conditional signal assignment (VHDL),
3. nested **if** statements,
4. **case** statement,
5. uses a selected signal assignment (VHDL).

All models synthesize to the same circuit as shown.

There is no incorrect modeling method, however using the **case** statement requires less code and is easier to read when compared with the **if** statement. This becomes more distinct with increasing inputs per output; see also Example 6.5. The two VHDL only models, 2 and 5, use concurrent signal assignments so reside outside a process. This means they are always active and so will usually take longer to simulate.

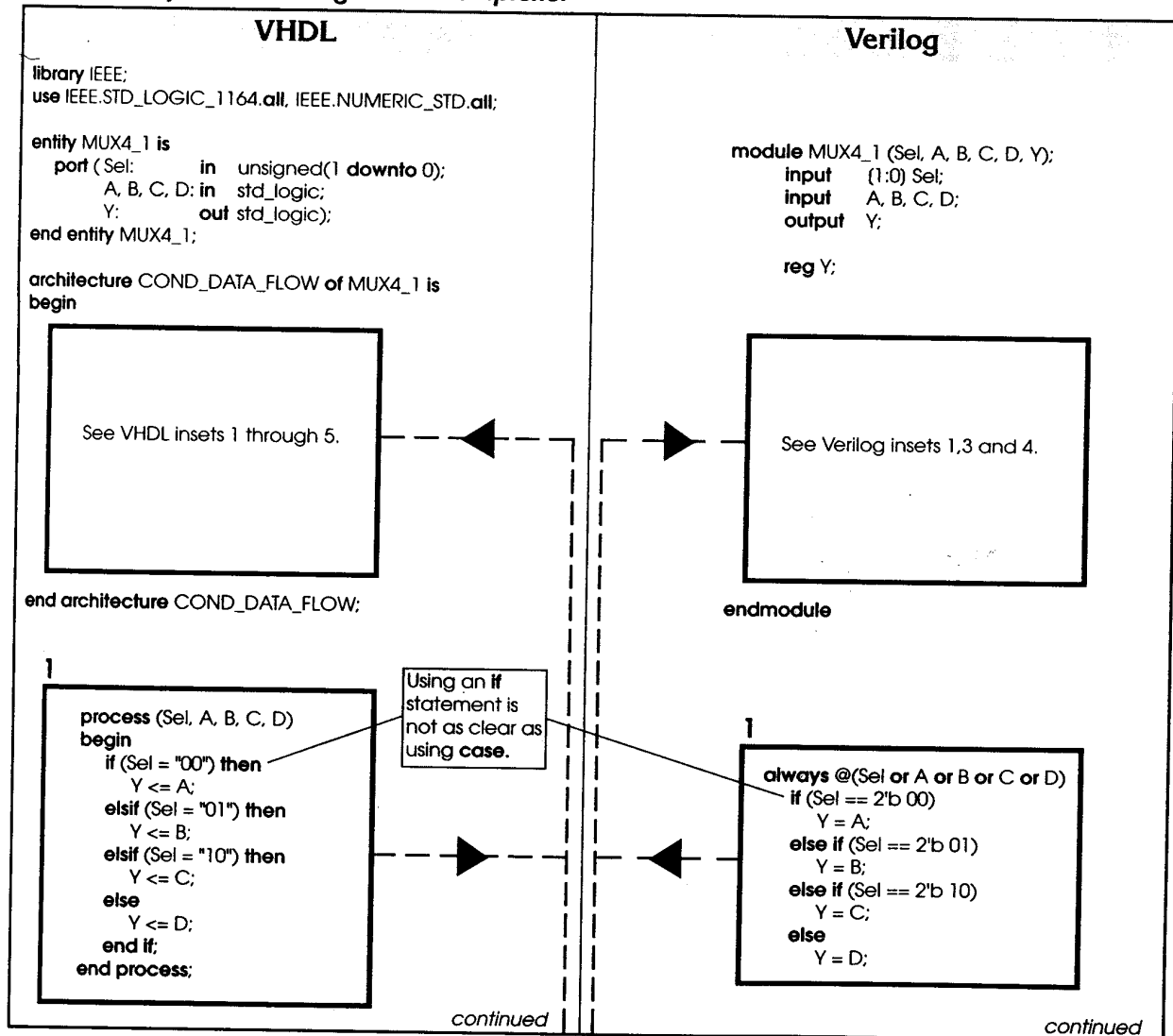**Different ways of modeling a 4-1 multiplexer**

## Different ways of modeling a 4-1 multiplexer

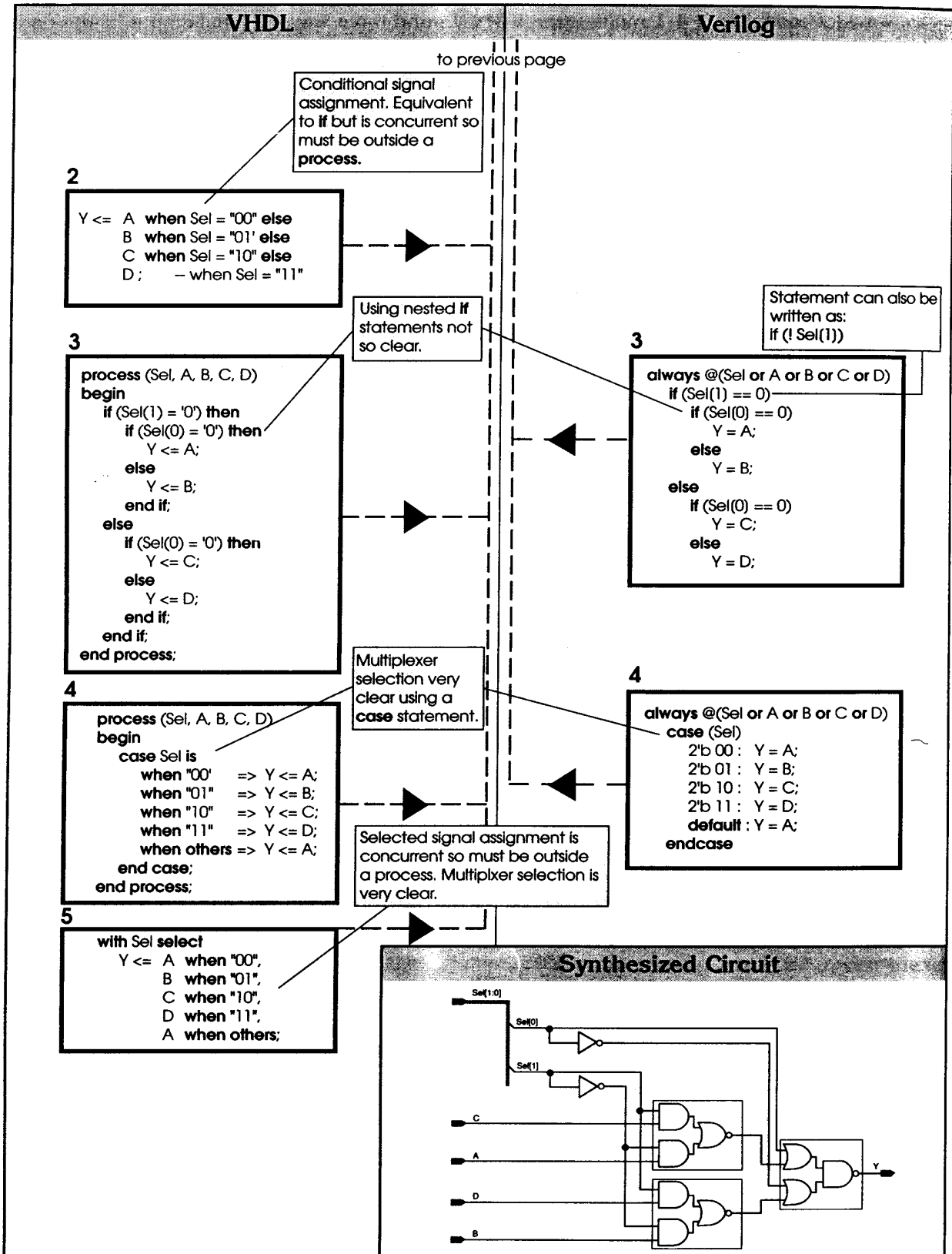



**Example 6.5 Two-bit wide 8-1 multiplexer using case**

A 2-bit wide 8-1 multiplexer is modeled to the truth table in Table 6.1. Models use the **case** statement, and additionally for VHDL only, selected signal assignment. The **if** statement becomes cumbersome for the wider inputs. It is different from the previous example in that a VHDL integer data type is used for the select input Sel, and the Verilog **case** selector values are specified in integer form, that is, 4 instead of 3'b 0100.

| Sel | A7 | A6 | A5 | A4 | A3 | A2 | A1 | A0 | Y  |
|-----|----|----|----|----|----|----|----|----|----|
| 000 | XX | XX | XX | XX | XX | XX | XX | DD | DD |
| 001 | XX | XX | XX | XX | XX | XX | DD | XX | DD |
| 010 | XX | XX | XX | XX | XX | DD | XX | XX | DD |
| 011 | XX | XX | XX | XX | DD | XX | XX | XX | DD |
| 100 | XX | XX | XX | DD | XX | XX | XX | XX | DD |
| 101 | XX | XX | DD | XX | XX | XX | XX | XX | DD |
| 110 | XX | DD | XX | XX | XX | XX | XX | XX | DD |
| 111 | DD | XX | XX | XX | XX | XX | XX | XX | DD |

XX = two bit don't care DD = two bit data


**Table 6.1 Truth table for a two bit wide 8-1 multiplexer**

**Two bit wide 8-1 multiplexer**

| VHDL  | Verilog   |
|---|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity MUX2X8_1_CASE is   port (Sel: in integer range 0 to 7;         A0,A1,A2,A3,A4,A5,A6,A7: in unsigned(1 downto 0);         Y: out unsigned(1 downto 0)); end entity MUX2X8_1_CASE; architecture COND_DATA_FLOW of MUX2X8_1_CASE is begin   process (Sel, A0, A1, A2, A3, A4, A5, A6, A7)   begin     case Sel is       when 0 =&gt; Y &lt;= A0;       when 1 =&gt; Y &lt;= A1;       when 2 =&gt; Y &lt;= A2;       when 3 =&gt; Y &lt;= A3;       when 4 =&gt; Y &lt;= A4;       when 5 =&gt; Y &lt;= A5;       when 6 =&gt; Y &lt;= A6;       when 7 =&gt; Y &lt;= A7;     end case;   end process; end architecture COND_DATA_FLOW; </pre> | <pre> module MUX2X8_1_CASE (Sel, A0, A1, A2, A3, A4, A5, A6, A7, Y);   input  (2:0) Sel;   input  (1:0) A0, A1, A2, A3, A4, A5, A6, A7;   output (1:0) Y;    reg [1:0] Y;    always @(Sel or A0 or A1 or A2 or            A3 or A4 or A5 or A6 or A7)   case (Sel)     0 : Y = A0;     1 : Y = A1;     2 : Y = A2;     3 : Y = A3;     4 : Y = A4;     5 : Y = A5;     6 : Y = A6;     7 : Y = A7;     default : Y = A0;   endcase endmodule </pre> |

| VHDL   |
|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity MUX2X8_1_SSA is   port (Sel: in integer range 0 to 7;         A0,A1,A2,A3,A4,A5,A6,A7: in unsigned(1 downto 0);         Y: out unsigned(1 downto 0)); end entity MUX2X8_1_SSA; architecture COND_DATA_FLOW of MUX2X8_1_SSA is begin   with Sel select     Y &lt;= A0 when 0,          A1 when 1,          A2 when 2,          A3 when 3,          A4 when 4,          A5 when 5,          A6 when 6,          A7 when 7; end architecture COND_DATA_FLOW; </pre> |

## Two-bit wide 8-1 multiplexer

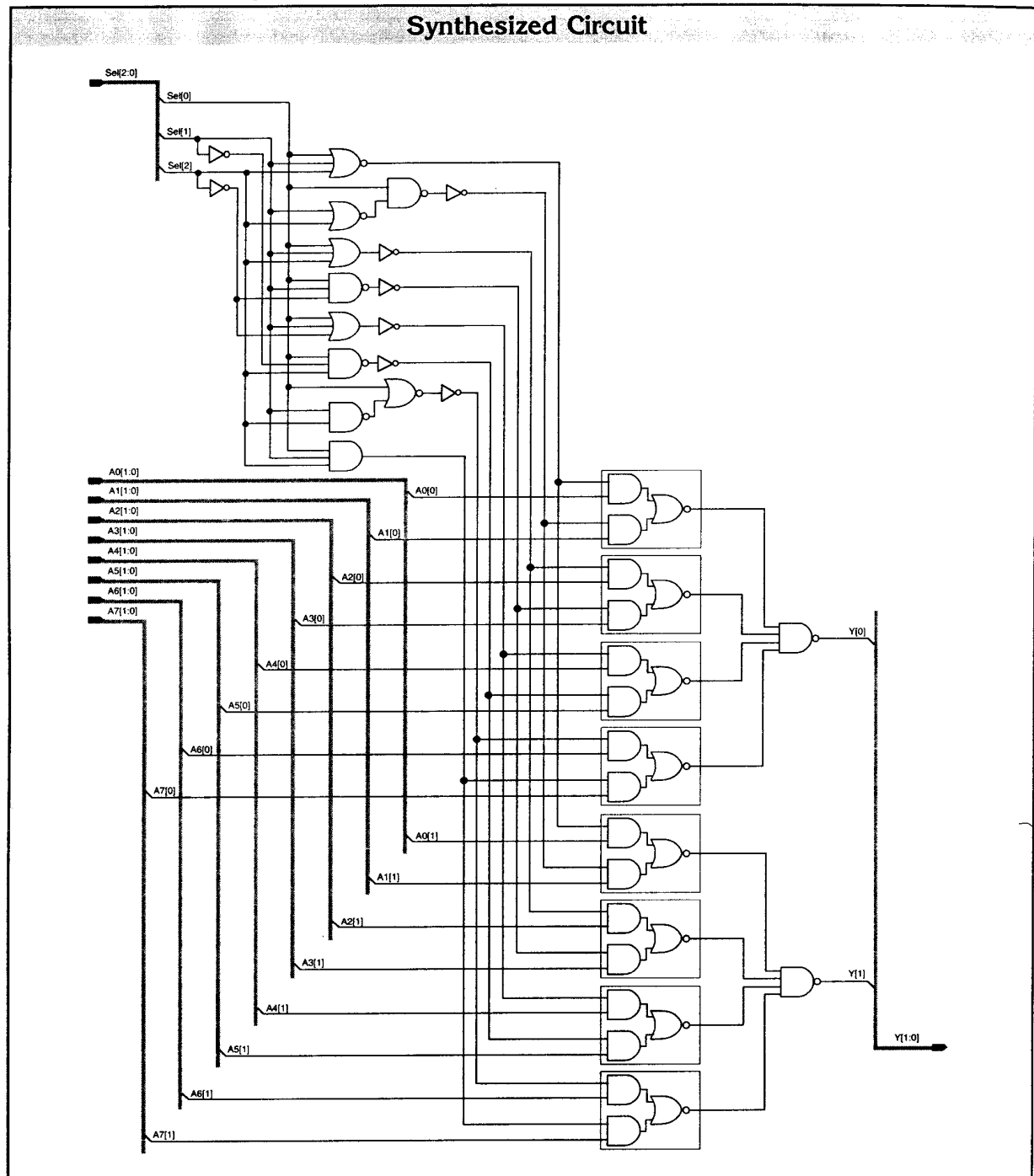

## Encoders

Discrete quantities of digital information, data, are often represented in a coded form; binary being the most popular. Encoders are used to encode discrete data into a coded form and decoders are used to convert it back into its original undecoded form. An encoder that has  $2^n$  (or less) input lines encodes input data to provide  $n$  encoded output lines. The truth table for an 8-3 binary encoder (8 inputs and 3 outputs) is shown in Table 6.2. It is assumed that only one input has a value of 1 at any given time, otherwise the output has some undefined value and the circuit is meaningless.

| inputs |    |    |    |    |    |    |    | outputs |    |    |
|--------|----|----|----|----|----|----|----|---------|----|----|
| A7     | A6 | A5 | A4 | A3 | A2 | A1 | A0 | Y2      | Y1 | Y0 |
| 0      | 0  | 0  | 0  | 0  | 0  | 0  | 1  | 0       | 0  | 0  |
| 0      | 0  | 0  | 0  | 0  | 0  | 1  | 0  | 0       | 0  | 1  |
| 0      | 0  | 0  | 0  | 0  | 1  | 0  | 0  | 0       | 1  | 0  |
| 0      | 0  | 0  | 0  | 1  | 0  | 0  | 0  | 0       | 1  | 1  |
| 0      | 0  | 0  | 1  | 0  | 0  | 0  | 0  | 1       | 0  | 0  |
| 0      | 0  | 1  | 0  | 0  | 0  | 0  | 0  | 1       | 0  | 1  |
| 0      | 1  | 0  | 0  | 0  | 0  | 0  | 0  | 1       | 1  | 0  |
| 1      | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 1       | 1  | 1  |

**Table 6.2 Truth table for an 8-3 binary encoder**

The truth table can be modeled using the **if**, **case** or **for** statements.

Models using a **case** statement are clearer than those using an **if** statement. The **for** loop is better for modeling a larger or more generic  $m$ - $n$  bit encoder. All models of such a circuit must use a default "don't care" value to minimize the synthesized circuit as only 8 of the 256 ( $2^8$ ) input conditions need to be specified. The synthesis tool, if capable, replaces "don't care" values with logic 0 or 1 values as necessary in order to minimize the circuit's logic. This means VHDL integer data type cannot be used for the case selector in a **case** statement. However, whatever data type is used, for example, unsigned, it can always be converted from an integer data type before the **case** statement and back again after, although this can be cumbersome.

Example 6.6 shows models of the 8-3 binary encoder described above, using either the **if**, **case** or **for** statement.

### Example 6.6 An 8-3 binary encoder

An 8-3 encoder is modeled according to the truth table of Table 6.2 using the **if**, **case** or **for** statement, and additionally for VHDL, conditional and selected signal assignments.

All models use a default assigned output value to avoid having to explicitly define all  $2^8 - 8 = 248$  input conditions that should not occur under normal operating conditions. The default assignment is a "don't care" value to minimize synthesized logic. If all 248 input conditions that are not explicitly defined default to binary 000, more logic would be synthesized than is necessary.

## 8-3 encoder modeled from the truth table

| VHDL   | Verilog   |
|--|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity ENCODE_8_3_IF_ELSE is   port ( A: in  unsigned(7 downto 0);         Y: out unsigned(2 downto 0)); end entity ENCODE_8_3_IF_ELSE;  architecture COND_DATA_FLOW of ENCODE_8_3_IF_ELSE is begin   process (A)   begin     if (A = "00000001") then Y &lt;= "000";     elsif (A = "00000010") then Y &lt;= "001";     elsif (A = "00000100") then Y &lt;= "010";     elsif (A = "00001000") then Y &lt;= "011";     elsif (A = "00010000") then Y &lt;= "100";     elsif (A = "00100000") then Y &lt;= "101";     elsif (A = "01000000") then Y &lt;= "110";     elsif (A = "10000000") then Y &lt;= "111";     else Y &lt;= "XXX";     end if;   end process; end architecture COND_DATA_FLOW; </pre> | <pre> module ENCODER_8_3_IF_ELSE (A, Y);   input  (7:0) A;   output (2:0) Y;    reg (2:0) Y;    always @(A)   begin     if (A == 8'b 00000001) Y = 0;     else if (A == 8'b 00000010) Y = 1;     else if (A == 8'b 00000100) Y = 2;     else if (A == 8'b 00001000) Y = 3;     else if (A == 8'b 00010000) Y = 4;     else if (A == 8'b 00100000) Y = 5;     else if (A == 8'b 01000000) Y = 6;     else if (A == 8'b 10000000) Y = 7;     else Y = 3'b X;   end endmodule </pre> |

| VHDL   |
|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity ENCODE_8_3_CSA is   port ( A: in  unsigned(7 downto 0);         Y: out unsigned(2 downto 0)); end entity ENCODE_8_3_CSA;  architecture LOGIC of ENCODE_8_3_CSA is begin   Y &lt;= "000" when A = "00000001" else         "001" when A = "00000010" else         "010" when A = "00000100" else         "011" when A = "00001000" else         "100" when A = "00010000" else         "101" when A = "00100000" else         "110" when A = "01000000" else         "111" when A = "10000000" else         "XXX"; end architecture LOGIC; </pre> <div data-bbox="694 1131 845 1310" style="border: 1px solid black; padding: 5px; margin-top: 10px;"> <p>Conditional signal assignment which is the concurrent equivalent of if statement.</p> </div> |

## 8-3 encoder modeled from the truth table (continued)


| VHDL  | Verilog  |
|---|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity ENCODE_8_3_CASE is   port ( A: in  unsigned(7 downto 0);         Y: out unsigned(2 downto 0)); end entity ENCODE_8_3_CASE;  architecture LOGIC of ENCODE_8_3_CASE is begin   process (A)   begin     case A is       when "00000001" =&gt; Y &lt;= "000";       when "00000010" =&gt; Y &lt;= "001";       when "00000100" =&gt; Y &lt;= "010";       when "00001000" =&gt; Y &lt;= "011";       when "00010000" =&gt; Y &lt;= "100";       when "00100000" =&gt; Y &lt;= "101";       when "01000000" =&gt; Y &lt;= "110";       when "10000000" =&gt; Y &lt;= "111";       when others      =&gt; Y &lt;= "XXX";     end case;   end process; end architecture LOGIC; </pre> | <pre> module ENCODE_8_3_CASE (A, Y);   input  (7:0) A;   output (2:0) Y;   reg (2:0) Y;    always @(A)   begin     caseX (A)       8'b 00000001 : Y = 0;       8'b 00000010 : Y = 1;       8'b 00000100 : Y = 2;       8'b 00001000 : Y = 3;       8'b 00010000 : Y = 4;       8'b 00100000 : Y = 5;       8'b 01000000 : Y = 6;       8'b 10000000 : Y = 7;       default :      Y = 3'b X;     endcase   end  endmodule </pre> |

case statement is very clear.

| VHDL   |
|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity ENCODE_8_3_SSA is   port ( A: in  unsigned(7 downto 0);         Y: out unsigned(2 downto 0)); end entity ENCODE_8_3_SSA;  architecture LOGIC of ENCODE_8_3_SSA is begin   with A select     Y &lt;= "000" when "00000001",          "001" when "00000010",          "010" when "00000100",          "011" when "00001000",          "100" when "00010000",          "101" when "00100000",          "110" when "01000000",          "111" when "10000000",          "XXX" when others; end architecture LOGIC; </pre> |

Selected signal assignment is also very clear. It is the concurrent equivalent of case statement.
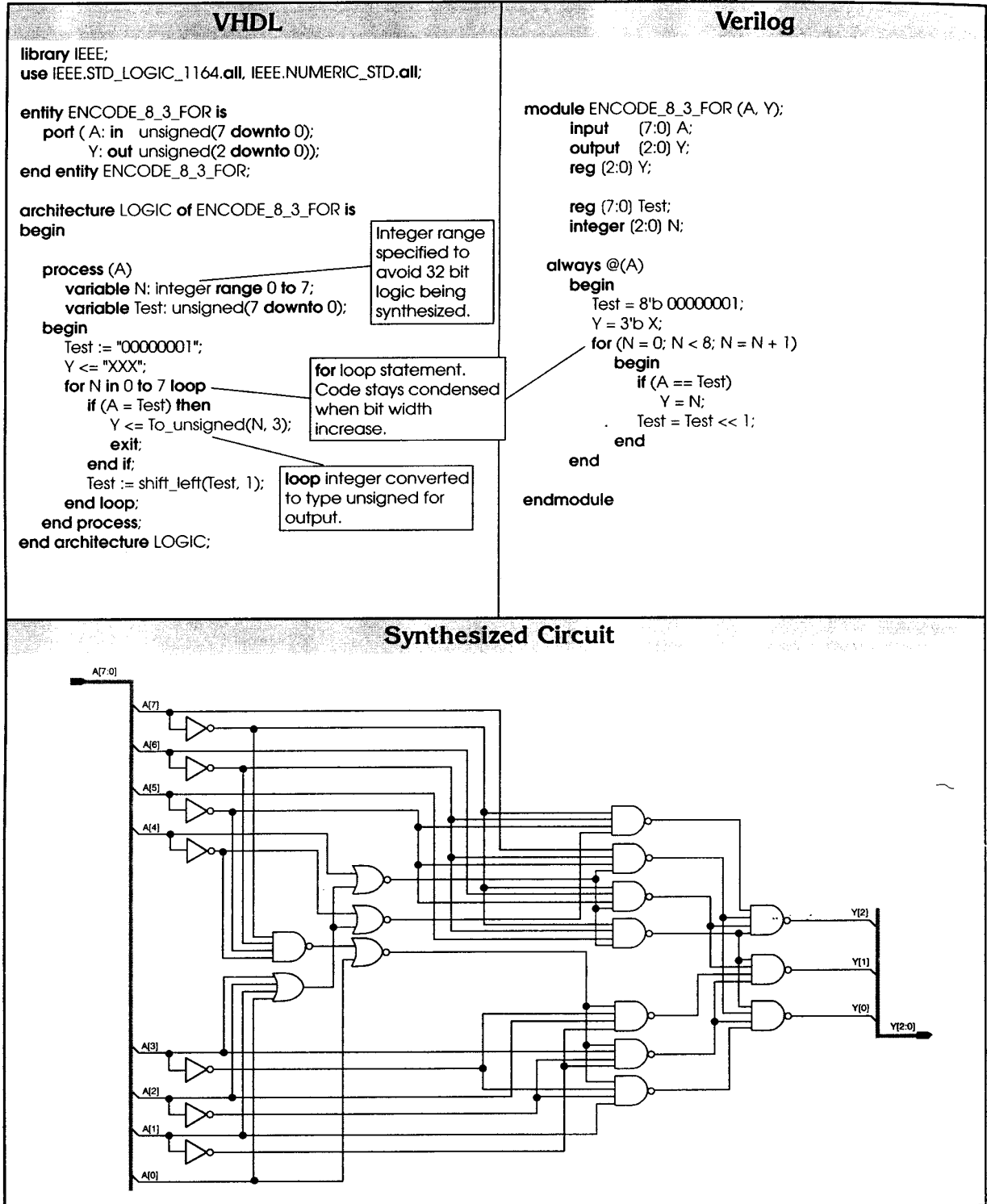
## 8-3 encoder modeled from the truth table (continued)



## Priority Encoders

The operation of the priority encoder is such that if two or more single bit inputs are at a logic 1, then the input with the highest priority will take precedence, and its particular coded value will be output. Models of an 8-3 binary priority encoder are included in Example 6.7.

### Example 6.7 An 8-3 binary priority encoder

An 8-3 priority encoder is modeled in several different ways to the truth table shown in Table 6.3. The most significant bit, A7, has the highest priority. The output signal Valid indicates that at least one input bit is at logic 1 and signifies the 3-bit output Y is valid.

Different models use **if**, **case** and **for** statements. They all use "don't care" default value for the 3-bit output Y for the condition when all 8 inputs are at logic 0. This gives the synthesis tool the potential to reduce the logic, although it makes little or no difference in this particular model.

*Using if statements.* The first model uses an **if** statement to test each bit in turn starting from the highest priority bit, A7.

| inputs |    |    |    |    |    |    |    | outputs |    |    |       |
|--------|----|----|----|----|----|----|----|---------|----|----|-------|
| A7     | A6 | A5 | A4 | A3 | A2 | A1 | A0 | Y2      | Y1 | Y0 | Valid |
| 0      | 0  | 0  | 0  | 0  | 0  | 0  | 0  | X       | X  | X  | 0     |
| 0      | 0  | 0  | 0  | 0  | 0  | 0  | 1  | 0       | 0  | 0  | 1     |
| 0      | 0  | 0  | 0  | 0  | 0  | 1  | X  | 0       | 0  | 1  | 1     |
| 0      | 0  | 0  | 0  | 0  | 1  | X  | X  | 0       | 1  | 0  | 1     |
| 0      | 0  | 0  | 0  | 1  | X  | X  | X  | 0       | 1  | 1  | 1     |
| 0      | 0  | 0  | 1  | X  | X  | X  | X  | 1       | 0  | 0  | 1     |
| 0      | 0  | 1  | X  | X  | X  | X  | X  | 1       | 0  | 1  | 1     |
| 0      | 1  | X  | X  | X  | X  | X  | X  | 1       | 1  | 0  | 1     |
| 1      | X  | X  | X  | X  | X  | X  | X  | 1       | 1  | 1  | 1     |

X = don't care


**Table 6.3 Truth table of an 8-3 binary priority encoder**

*Using case/casex statements.* The second model uses a VHDL **case** statement and Verilog **casex** statement. The Verilog **casex** statement is ideally suited for this model as it allows "don't care" input conditions to be used. The VHDL **case** statement is not suitable at all, and the only practical way of using it is to convert signal A from an unsigned to integer data type and specify the appropriate range or each choice value. This type of model will typically cause a synthesis tool to generate large amounts of redundant logic which must then be optimized away by the optimizer. In this particular sized model the optimizer is able to produce identical circuits. However, this may not be the case for larger priority encoders due to the heuristic nature of logic optimizers.

*Using conditional signal assignments (VHDL).* If the priority encoder was modeled using VHDL conditional signal assignments, two assignments would be needed; one for each output, Valid and Y. Each assignment would be similar in that they would separately select each value of the input A. The synthesized circuit would also be the same, but there would be code duplication for the input selection. This results in more code that is less comprehensible. It is not recommended, and not shown in this example.


*Using for loop statements.* The third model uses the **for** loop and tests each bit in turn. The advantage is that the code does not get progressively larger as input and output bit widths increase. Default output values are defined before the **for** statement. There are two VHDL versions; the first checks each bit in turn starting from the least LSB, the second checks each bit in turn starting from the MSB and exits the loop when it has found the first bit having a logic 1 value.
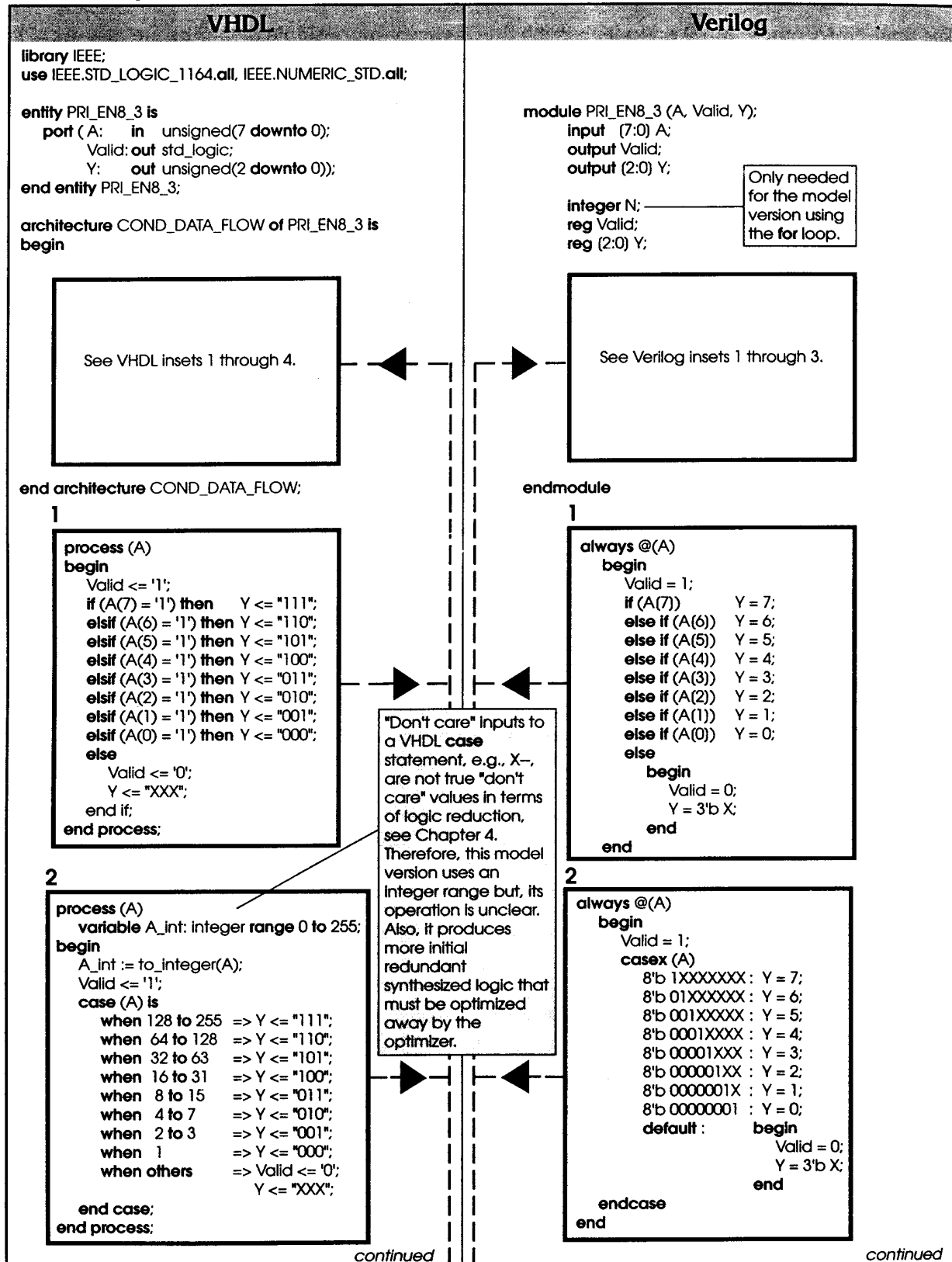
## Different ways of modeling an 8-3 priority encoder




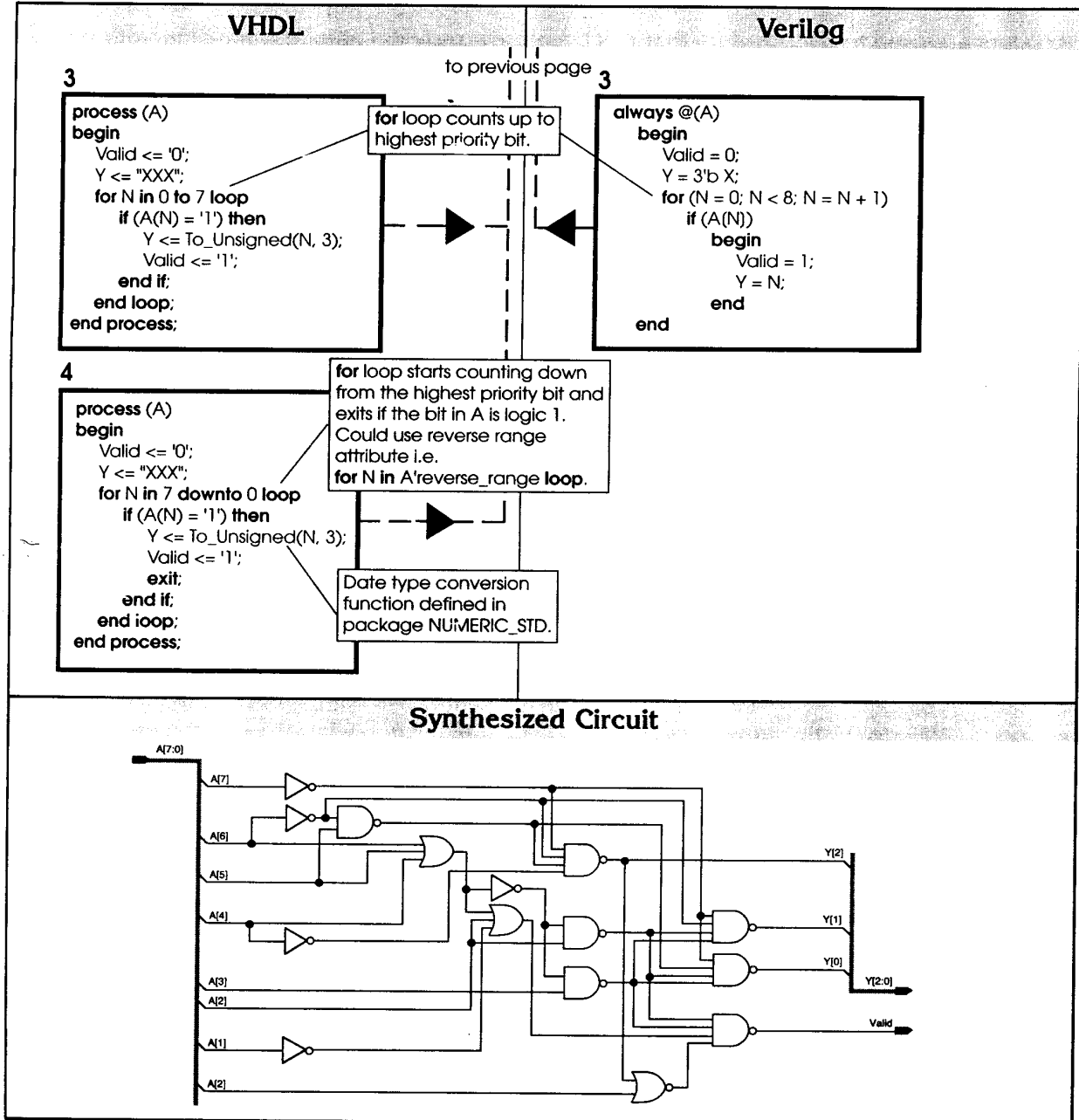
## Different ways of modeling an 8-3 priority encoder



## Decoders

Decoders are used to decode data that has been previously encoded using a binary, or possibly other, type of coded format. An  $n$ -bit code can represent up to  $2^n$  distinct bits of coded information, so a decoder with  $n$  inputs can decode up to  $2^n$  outputs. Various models of a 3-8 binary decoder are included in Example 6.8, while various models of a 3-6 binary decoder having a separate enable input are included in Example 6.9.

### Example 6.8 A 3-8 binary decoder


The models of a 3-8 binary decoder in this example conform to the truth table in Table 6.4.

Different model versions use **if**, **case** and **for** statements along with VHDL conditional and selected signal assignments. All  $2^3 = 8$  possible input values of this 3-8 decoder are decoded to a unique output. This means the automatic priority encoding employed by **if** and Verilog **case** statements do not affect the circuit and "don't care" output values are not needed. Like most other examples in this chapter there is no right or wrong modeling technique. The **case** statement is commonly used because of its clarity, and the fact it is not a continuous assignment and so may simulate faster. As input and output bit widths increase, it is more code efficient to use the **for** loop statement. Again, all models synthesize to the same circuit.


| inputs |    |    | outputs |    |    |    |    |    |    |    |
|--------|----|----|---------|----|----|----|----|----|----|----|
| A2     | A1 | A0 | Y7      | Y6 | Y5 | Y4 | Y3 | Y2 | Y1 | Y0 |
| 0      | 0  | 0  | 0       | 0  | 0  | 0  | 0  | 0  | 0  | 1  |
| 0      | 0  | 1  | 0       | 0  | 0  | 0  | 0  | 0  | 1  | 0  |
| 0      | 1  | 0  | 0       | 0  | 0  | 0  | 0  | 1  | 0  | 0  |
| 0      | 1  | 1  | 0       | 0  | 0  | 0  | 1  | 0  | 0  | 0  |
| 1      | 0  | 0  | 0       | 0  | 0  | 1  | 0  | 0  | 0  | 0  |
| 1      | 0  | 1  | 0       | 0  | 1  | 0  | 0  | 0  | 0  | 0  |
| 1      | 1  | 0  | 0       | 1  | 0  | 0  | 0  | 0  | 0  | 0  |
| 1      | 1  | 1  | 1       | 0  | 0  | 0  | 0  | 0  | 0  | 0  |

**Table 6.4 Truth table for a 3-8 line binary decoder**
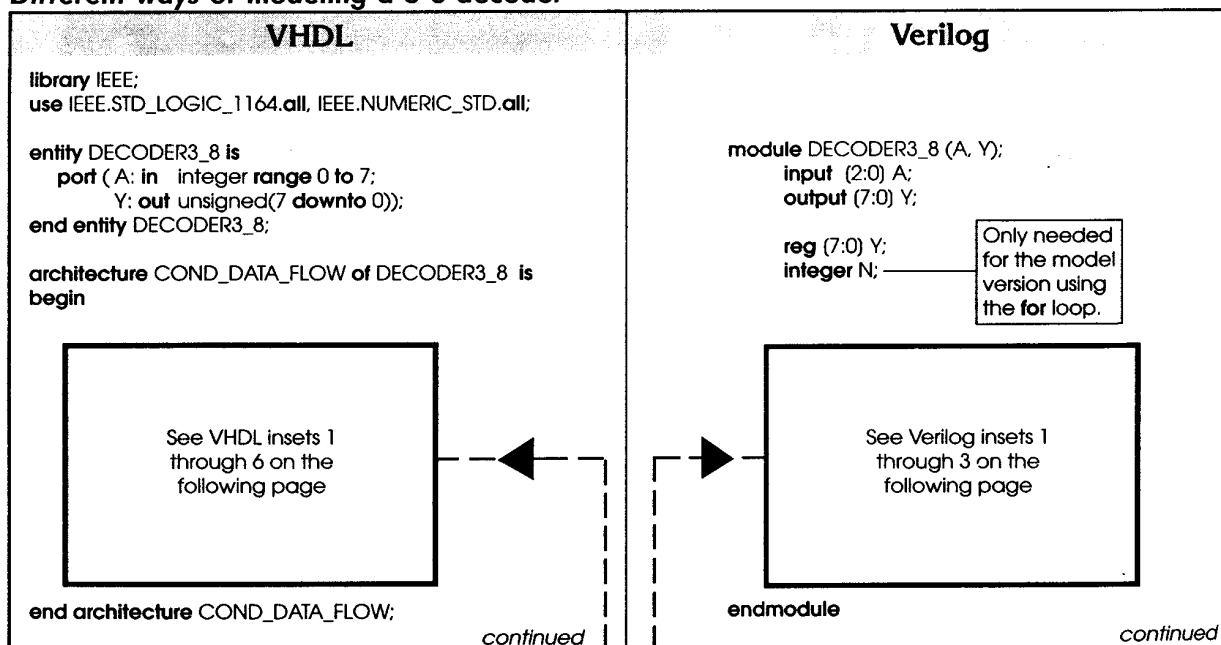
### Different ways of modeling a 3-8 decoder



## Different ways of modeling an 3-8 decoder

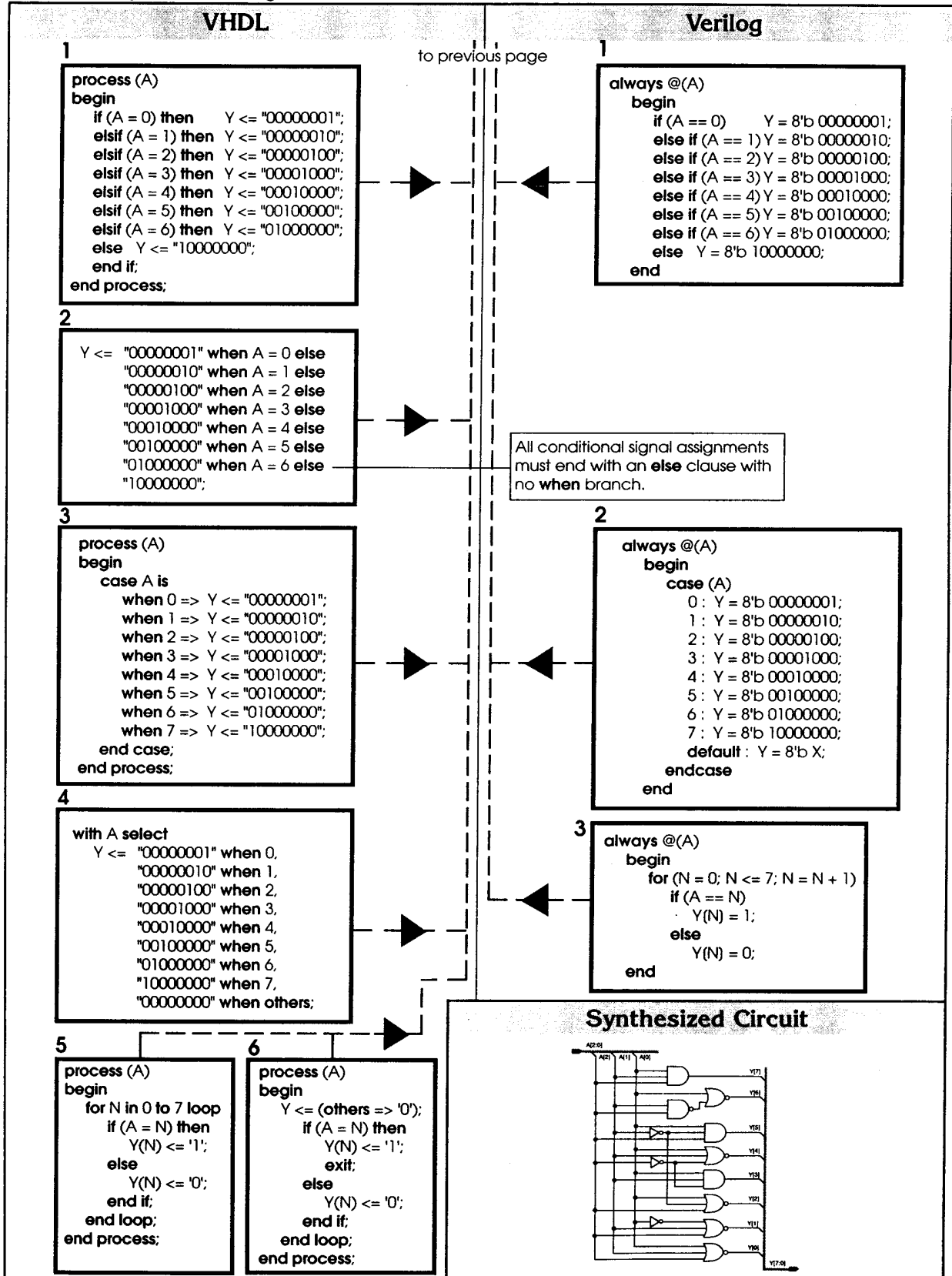

**Example 6.9 A 3-6 binary decoder with enable**

The two model versions of a 3-6 binary decoder are included in this example and conform to the truth table; Table 6.5. Because of the similarities of this example to Example 6.8, only the versions using a **case** statement are covered. This example is different because it has a separate input enable signal and there are two unused binary values for the 3-bit input A. When the enable is inactive ( $En = 0$ ), or A has an unused value, the 6-bit output must be at logic 0. Like the previous example, "don't care" default assigned values cannot be used.

| En | inputs |    |    | outputs |    |    |    |    |    |
|----|--------|----|----|---------|----|----|----|----|----|
|    | A2     | A1 | A0 | Y5      | Y4 | Y3 | Y2 | Y1 | Y0 |
| 0  | X      | X  | X  | 0       | 0  | 0  | 0  | 0  | 0  |
| 1  | 0      | 0  | 0  | 0       | 0  | 0  | 0  | 0  | 1  |
| 1  | 0      | 0  | 1  | 0       | 0  | 0  | 0  | 1  | 0  |
| 1  | 0      | 1  | 0  | 0       | 0  | 0  | 1  | 0  | 0  |
| 1  | 0      | 1  | 1  | 0       | 0  | 1  | 0  | 0  | 0  |
| 1  | 1      | 0  | 0  | 0       | 1  | 0  | 0  | 0  | 0  |
| 1  | 1      | 0  | 1  | 1       | 0  | 0  | 0  | 0  | 0  |
| 1  | 1      | 1  | 0  | 0       | 0  | 0  | 0  | 0  | 0  |
| 1  | 1      | 1  | 1  | 0       | 0  | 0  | 0  | 0  | 0  |
| 1  | 1      | 1  | 1  | 0       | 0  | 0  | 0  | 0  | 0  |

X=don't care

**Table 6.5 Truth table for a 3-6 line binary decoder with enable**

The first model version below also uses an **if** statement to check the enable input  $En$ , separately from the enclosed **case** statement. The second version on the following page has the enable input  $En$ , concatenated with the encoded input A and the combined signal used in the **case** statement. Both are correct and synthesize to the same circuit as shown.

**3-6 decoder with separate if branch which tests the enable input**

| VHDL  | Verilog  |
|---|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity DECODER3_6_CASE1 is     port ( En: in  std_logic;           A: in  integer range 0 to 7;           Y: out unsigned(5 downto 0)); end entity DECODER3_6_CASE1;  architecture COND_DATA_FLOW of DECODER3_6_CASE1 is begin     process (A)     begin         if (En = '0') then             Y &lt;= "000000";         else             case A is                 when 0 =&gt; Y &lt;= "000001";                 when 1 =&gt; Y &lt;= "000010";                 when 2 =&gt; Y &lt;= "000100";                 when 3 =&gt; Y &lt;= "001000";                 when 4 =&gt; Y &lt;= "010000";                 when 5 =&gt; Y &lt;= "100000";                 when others =&gt; Y &lt;= "000000";             end case;         end if;     end process; end architecture COND_DATA_FLOW; </pre> | <pre> module DECODER3_6_CASE1 (A, En, Y);     input En;     input [2:0] A;     output [5:0] Y;      reg [5:0] Y;      always @(En or A)     begin         if (!En)             Y = 6'b 0;         else             case (A)                 0: Y = 6'b 000001;                 1: Y = 6'b 000010;                 2: Y = 6'b 000100;                 3: Y = 6'b 001000;                 4: Y = 6'b 010000;                 5: Y = 6'b 100000;                 default: Y = 6'b 0;             endcase         end     end endmodule </pre> |


## 3-6 decoder with concatenated enable/encoded input for case selector

| VHDL   | Verilog  |
|--|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity DECODER3_6_CASE2 is   port ( En: in  std_logic;         A: in  unsigned(2 downto 0);         Y: out unsigned(5 downto 0)); end entity DECODER3_6_CASE2;  architecture COND_DATA_FLOW of DECODER3_6_CASE2 is begin   process (En, A)     variable En_concat_A: unsigned(3 downto 0);   begin     En_concat_A := En &amp; A;     case En_concat_A is       when "1000" =&gt; Y &lt;= "000001";       when "1001" =&gt; Y &lt;= "000010";       when "1010" =&gt; Y &lt;= "000100";       when "1011" =&gt; Y &lt;= "001000";       when "1100" =&gt; Y &lt;= "010000";       when "1101" =&gt; Y &lt;= "100000";       when others =&gt; Y &lt;= "000000";     end case;   end process; end architecture COND_DATA_FLOW; </pre> | <pre> module DECODER3_6_CASE2 (A, En, Y);   input En;   input [2:0] A;   output [5:0] Y;    reg [3:0] En_concat_A;   reg [5:0] Y;    always @(En or A)   begin     case ({En, A})       4'b 1000 : Y = 6'b 000001;       4'b 1001 : Y = 6'b 000010;       4'b 1010 : Y = 6'b 000100;       4'b 1011 : Y = 6'b 001000;       4'b 1100 : Y = 6'b 010000;       4'b 1101 : Y = 6'b 100000;       default  : Y = 6'b 0;     endcase   end endmodule </pre> |

Separate concatenation expression. Not allowed in **case** expression like Verilog.


Concatenation in **case** expression.

## Synthesized Circuit

 

### Example 6.10 Four bit address decoder

This example is of a four bit address decoder. It provides enable signals for segments of memory, the address map of which, is shown in Figure 6.3. The decoder's inputs could be the upper four bits of a larger address bus in which case the decoded outputs would enable larger segments of memory. Seven enable outputs are provided; one for each memory segment. The address map is divided into quarters, and the second quarter is further subdivided into four. There are four outputs from the second quarter corresponding to four consecutive binary input values.

 

**Figure 6.3**  
**Address map**

The first model version uses a **for** loop enclosing an **if** statement while the second model uses a **case** statement. As a general rule, it is better to use the **for** loop and **if** statements when a large number of consecutively decoded outputs are required. This is because a **case** statement requires a separate choice branch for each decoded output.


#### Four bit address decoder using "if" in a "for" loop

| VHDL   | Verilog  |
|--|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity ADD_DEC_IF is     port ( Address: in  integer range 0 to 15;           AddDec_0to3, AddDec_8to11,           AddDec_12to15: out std_logic;           AddDec_4to7: out unsigned(3 downto 0)); end entity ADD_DEC_IF; architecture COND_DATA_FLOW of ADD_DEC_IF is begin     process (Address)     begin         -- First quarter         if (Address &gt;= 0 and Address &lt;= 3) then             AddDec_0to3 &lt;= '1';         else             AddDec_0to3 &lt;= '0';         end if;          -- Third quarter         if (Address &gt;= 8 and Address &lt;= 11) then             AddDec_8to11 &lt;= '1';         else             AddDec_8to11 &lt;= '0';         end if;          -- Fourth quarter         if (Address &gt;= 12 and Address &lt;= 15) then             AddDec_12to15 &lt;= '1';         else             AddDec_12to15 &lt;= '0';         end if;          -- Second quarter         for N in AddDec_4to7'range loop             if (Address = N + 4) then                 AddDec_4to7(N) &lt;= '1';             else                 AddDec_4to7(N) &lt;= '0';             end if;         end loop;     end process; end architecture COND_DATA_FLOW; </pre> | <pre> module ADD_DEC_IF     (Address, AddDec_0to3, AddDec_4to7,      AddDec_8to11, AddDec_12to15);     input  (3:0)  Address;     output      AddDec_0to3, AddDec_8to11,                AddDec_12to15;     output (3:0) AddDec_4to7;     integer N;     reg AddDec_0to3, AddDec_8to11,        AddDec_12to15;     reg (3:0) AddDec_4to7;     always @(Address)     begin         // First quarter         if (Address &gt;= 0 &amp;&amp; Address &lt;= 3)             AddDec_0to3 = 1;         else             AddDec_0to3 = 0;          // Third quarter         if (Address &gt;= 8 &amp;&amp; Address &lt;= 11)             AddDec_8to11 = 1;         else             AddDec_8to11 = 0;          // Fourth quarter         if (Address &gt;= 12 &amp;&amp; Address &lt;= 15)             AddDec_12to15 = 1;         else             AddDec_12to15 = 0;          // Second quarter         for (N = 0; N &lt;= 3; N = N + 1)             if (Address == N + 4)                 AddDec_4to7(N) = 1;             else                 AddDec_4to7(N) = 0;         end     end endmodule </pre> |

## Four bit address decoder using "case"

| VHDL   | Verilog   |
|--|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity ADD_DEC_CASE is   port ( Address:      in  integer range 0 to 15;         AddDec_0to3, AddDec_8to11,         AddDec_12to15: out std_logic;         AddDec_4to7:   out unsigned(3 downto 0)); end entity ADD_DEC_CASE;  architecture COND_DATA_FLOW of ADD_DEC_CASE is begin    process (Address)   begin     AddDec_0to3   &lt;= '0';     AddDec_4to7   &lt;= (others =&gt; '0');     AddDec_8to11  &lt;= '0';     AddDec_12to15 &lt;= '0';      case Address is       -- First quarter       when 0 to 3 =&gt;         AddDec_0to3 &lt;= '1';        -- Second quarter       when 4 =&gt; AddDec_4to7(0) &lt;= '1';       when 5 =&gt; AddDec_4to7(1) &lt;= '1';       when 6 =&gt; AddDec_4to7(2) &lt;= '1';       when 7 =&gt; AddDec_4to7(3) &lt;= '1';        -- Third quarter       when 8 to 11 =&gt;         AddDec_8to11 &lt;= '1';        -- Fourth quarter       when 12 to 15 =&gt;         AddDec_12to15 &lt;= '1';     end case;   end process; end architecture COND_DATA_FLOW; </pre> | <pre> module ADD_DEC_CASE   (Address, AddDec_0to3, AddDec_4to7, AddDec_8to11,    AddDec_12to15);   input  (3:0)  Address;   output       AddDec_0to3, AddDec_8to11,              AddDec_12to15;   output (3:0)  AddDec_4to7;    reg AddDec_0to3, AddDec_8to11, AddDec_12to15;   reg (3:0) AddDec_4to7;    always @(Address)   begin     AddDec_0to3   = 0;     AddDec_4to7   = 0;     AddDec_8to11  = 0;     AddDec_12to15 = 0;      case (Address)       // First quarter       0, 1, 2, 3:         AddDec_0to3 = 1;        // Second quarter       4: AddDec_4to7(0) = 1;       5: AddDec_4to7(1) = 1;       6: AddDec_4to7(2) = 1;       7: AddDec_4to7(3) = 1;        // Third quarter       8, 9, 10, 11:         AddDec_8to11 = 1;        // Fourth quarter       12, 13, 14, 15:         AddDec_12to15 = 1;     endcase   end endmodule </pre> |

## Synthesized Circuit

 

**Example 6.11 Generic N to M bit binary decoder**

A generic  $n$ -bit input,  $m$ -bit output binary decoder is illustrated and incorporates a separate enable input. Like Example 6.9, all outputs will be at logic 0 if the decoder is not enabled, that is,  $En = 0$ , or it is enabled, but  $n$  has a value that is not used in the decoder. This generic decoder is called twice for the inference of a 2-4 and a 3-6 decoder.

The four models in this example are:

- VHDL 1 - a generic VHDL decoder using an **entity**,
- Verilog 1 - a generic Verilog decoder using a **module**,
- VHDL 2 - a generic VHDL decoder using a function in a package,
- Verilog 2 - non-generic Verilog using a decoder function Verilog 2.

There are two parts to each of the four models. The first part of VHDL 1 and Verilog 1 show the decoder model while the second part shows two separate instantiations of it. The first part of VHDL 2 and Verilog 2 show the decoder modeled in a function and the second part shows two function calls to it.

*VHDL 1.* Modeled using an **entity statement** and separately instantiated. The number of decoded input and output lines, needed for any given instance, are specified using a generic clause which specifies a value for `SizeIn` and `SizeOut`.

*Verilog 1.* Modeled using a **module statement** and instantiated from a separate module. Uses overloaded parameters for both input and output bit widths. These parameters have values defined for them in the generic decoder (`SizeIn = 3` and `SizeOut = 8`), and overridden when instantiated from the instantiation in another **module**.

*VHDL 2.* Uses a generic function defined in a package. This is a more practical and easier method to use when compared with using a VHDL **entity** as described above. The function is called from an expression, either concurrently (outside a process) or sequentially (inside a process), by supplying;

- the enable input of type `std_logic`,
- the encoded input of type `unsigned`,
- the desired number of encoded inputs of type `integer`,
- the desired number of decoded outputs of type `integer`.

*Verilog 2.* The Verilog language does not support the overriding of parameters in a function call. Instead of being able to model a generic decoder, a predefined number of  $n$ - $m$  bit decoders must be specified so that the appropriate decoder may be called when needed. In this version, two functions have been declared for 2-4 and 3-6 decoders. These decoders have been placed in a separate file and included in the calling **module** using the compiler directive `'include`.



**Generic decoder (entity/module)**

| VHDL 1  | Verilog 1   |
|---|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity GENERIC_DECODER_ENTITY is   generic (SizeIn, SizeOut: integer);   port (En: in std_logic;         A: in unsigned(SizeIn - 1 downto 0);         Y: out unsigned(SizeOut - 1 downto 0)); end entity GENERIC_DECODER_ENTITY;  architecture DATA_FLOW of GENERIC_DECODER_ENTITY is begin    process (En, A)   begin     if (En = '0') then       Y &lt;= (others =&gt; '0');     else       for N in 0 to SizeOut - 1 loop         if (to_integer(A) = N) then           Y(N) &lt;= '1';         else           Y(N) &lt;= '0';         end if;       end loop;     end if;   end process;  end architecture DATA_FLOW; </pre> | <pre> module GENERIC_DECODER_MODULE (En, A, Y);   parameter SizeIn = 3,              SizeOut = 8;   input      En;   input      [SizeIn - 1:0] A;   output     [SizeOut - 1:0] Y;   reg [SizeOut - 1:0] Y;    integer N;    always @(En or A)   begin     if (!En)       Y = 0;     else       if (A &gt; SizeOut - 1)         for (N = 0; N &lt;= SizeOut - 1; N = N + 1)           Y[N] = 1'b X;       else         for (N = 0; N &lt;= SizeOut - 1; N = N + 1)           if (A == N)             Y[N] = 1;           else             Y[N] = 0;           end if;         end for;       end if;     end if;   end  endmodule </pre> |

**Two instantiations of the generic decoder**

| VHDL 1  | Verilog 1   |
|---|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  entity GENERIC_DECODER_ENTITY_CALL is   port (EnA, EnB: in std_logic;         AddA: in unsigned(1 downto 0);         AddB: in unsigned(2 downto 0);         DecAddA: out unsigned(3 downto 0);         DecAddB: out unsigned(5 downto 0)); end entity GENERIC_DECODER_ENTITY_CALL;  architecture STRUCT of GENERIC_DECODER_ENTITY_CALL is   component GENERIC_DECODER_ENTITY     generic (SizeIn, SizeOut: integer);     port (En: in std_logic;           A: in unsigned(SizeIn - 1 downto 0);           Y: out unsigned(SizeOut - 1 downto 0));   end component; begin    Decoder2_4: GENERIC_DECODER_ENTITY     generic map (2, 4)     port map (EnA, AddA, DecAddA);    Decoder3_6: GENERIC_DECODER_ENTITY     generic map (3, 6)     port map (EnB, AddB, DecAddB);  end architecture STRUCT; </pre> | <pre> module GENERIC_DECODER_MODULE_CALL   (EnA, EnB, AddA, AddB, DecAddA, DecAddB);   input      EnA, EnB;   input      [1:0] AddA;   input      [2:0] AddB;   output     [3:0] DecAddA;   output     [5:0] DecAddB;    GENERIC_DECODER_MODULE     #(2, 4) Decoder2_4(EnA, AddA, DecAddA);    GENERIC_DECODER_MODULE     #(3, 6) Decoder3_6(EnB, AddB, DecAddB);  endmodule </pre> |

Two instantiations, 2-4 and 3-6, of the generic decoder.

## VHDL generic decoder (function) - Verilog specific decoders (functions)

| VHDL 2   | Verilog 2   |
|--|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  package GENERIC_DECODER_FN_PKG is   function Decoder (En: std_logic;                    A: unsigned;                    SizeIn, SizeOut: integer) return unsigned; end GENERIC_DECODER_FN_PKG;  package body GENERIC_DECODER_FN_PKG is   function Decoder (En: std_logic;                    A: unsigned;                    SizeIn, SizeOut: integer) return unsigned is     variable Y: unsigned(Size - 1 downto 0);   begin     if (En = '0' or A &gt; Size - 1) then       Y := (others =&gt; '0');     else       for N in 0 to SizeOut - 1 loop         if (to_integer(A) = N) then           Y(N) := '1';         else           Y(N) := '0';         end if;       end loop;     end if;     return Y;   end Decoder; end GENERIC_DECODER_FN_PKG; </pre> <p>Generic decoder function defined in a package.</p> | <pre> // ----- // This file must be called "decoder_fns.v". // ----- function (3:0) Decode2_4;   input En;   input (1:0) A;   integer N; begin   if (!En)     Decode2_4 = 4'b 0;   else     for (N = 0; N &lt; 4; N = N + 1)       if (A == N)         Decode2_4(N) = 1;       else         Decode2_4(N) = 0;     end   endfunction  function (5:0) Decode3_6;   input En;   input (2:0) A;   integer N; begin   if (!En)     Decode3_6 = 6'b 0;   else     for (N = 0; N &lt; 6; N = N + 1)       if (A == N)         Decode3_6(N) = 1;       else         Decode3_6(N) = 0;     end   endfunction endfunction </pre> <p>Two specific decoder functions.</p> |

## Two decoder function calls

| VHDL 2  | Verilog 2  |
|---|--|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all;  use work.GENERIC_DECODER_PKG.all;  entity GENERIC_DECODER_CALL_FN is   port ( EnA, EnB: in std_logic;          AddA: in unsigned(1 downto 0);          AddB: in unsigned(2 downto 0);          DecAddA: out unsigned(3 downto 0);          DecAddB: out unsigned(5 downto 0)); end entity GENERIC_DECODER_CALL_FN;  architecture DATA_FLOW of GENERIC_DECODER_CALL_FN is   begin     process (EnA, AddA, EnB, AddB)     begin       DecAddA &lt;= Decoder(EnA, AddA, 2, 4);       DecAddB &lt;= Decoder(EnB, AddB, 3, 6);     end process;   end architecture DATA_FLOW; </pre> <p>Two function calls to the generic decoder.</p> | <pre> module DECODER_FN_CALLS   (EnA, EnB, AddA, AddB, DecAddA, DecAddB);   input EnA, EnB;   input (1:0) AddA;   input (2:0) AddB;   output (3:0) DecAddA;   output (5:0) DecAddB;    reg (3:0) DecAddA;   reg (5:0) DecAddB;    `include "decoder_fns.v"    always @(EnA or EnB or AddA or AddB)   begin     DecAddA = Decode2_4(EnA, AddA);     DecAddB = Decode3_6(EnB, AddB);   end endmodule </pre> <p>Function calls to 2_4 and 3_6 decoders.</p> |

## Comparators

A comparator compares two or more inputs using one, or a number of different comparisons. When the given relationship(s) is true, an output signal is given (logic 0 or logic 1). Comparators are only modeled using the **if** statement with an **else** clause and no **else-if** clauses. A VHDL conditional signal assignment or Verilog conditional continuous assignment could also be used, but is less common as a sensitivity list (VHDL) or event list (Verilog) cannot be specified to improve simulation time. Any two data objects are compared using equality and relational

| Operators             | VHDL | Verilog |
|-----------------------|------|---------|
| Equality & Relational | =    | ==      |
|                       | !=   | !=      |
|                       | <    | <       |
|                       | <=   | <=      |
|                       | >    | >       |
| Logical               | >=   | >=      |
|                       | not  | !       |
|                       | and  | &&      |
|                       | or   |         |

operators in the expression part of the **if** statement. Only two data objects can be compared at once, that is, statements like "if (A = B = C)" cannot be used. However, logical operators can be used to logically test the result of multiple comparisons, for example, **if ((A = B) and (A = C))**. These equality, relational and logical operators are listed in Table 6.6.

Example 6.12 shows a 6-bit two input equality comparator. Example 6.13 shows how multiple comparisons are used.

**Table 6.6 Equality, relational and logical operators**

### Example 6.12 Simple Comparator

Identical equality comparators are shown coded in three different ways. The single bit output is at logic 1 when the two 6-bit input busses are the same, otherwise it is at logic 0.

#### Three ways to infer a 6-bit equality comparator

| VHDL  | Verilog  |
|---|--|
| <pre> library IEEE; use IEEE.STD_Logic_1164.all, IEEE.Numeric_STD.all; entity COMPARETOR_EQUALITY is   port (A1,B1,A2,B2,A3,B3: in unsigned(5 downto 0);         Y1, Y2, Y3: out std_logic); end entity COMPARETOR_EQUALITY; architecture LOGIC of COMPARETOR_EQUALITY is begin   COMPARE:   process (A1, B1, A2, B2, A3, B3)   begin     Y1 &lt;= '1';     for N in 0 to 5 loop       if (A1(N) /= B1(N)) then         Y1 &lt;= '0';         exit;       else         null;       end if;     end loop;     Y2 &lt;= '0';     if (A2 = B2) then       Y2 &lt;= '1';     end if;     if (A3 = B3) then       Y3 &lt;= '1';     else       Y3 &lt;= '0';     end if;   end process; end architecture LOGIC; </pre> | <pre> module COMPARETOR_EQUALITY (A1, B1, A2, B2, A3, B3, Y1, Y2, Y3); input (5:0) A1, B1, A2, B2, A3, B3; output Y1, Y2, Y3;  integer N; reg Y1, Y2, Y3;  always @(A1 or B1 or A2 or B2 or A3 or B3) begin: COMPARE   Y1 = 1;   for (N = 0; N &lt; 6; N = N + 1)     if (A1(N) != B1(N))       Y1 = 0;     else       ;   end   Y2 = 0;   if (A2 == B2)     Y2 = 1;   if (A3 == B3)     Y3 = 1;   else     Y3 = 0; end endmodule </pre> |


Each bit compared in turn in a for loop.

Default defined before the if so no else clause.

Most common and easiest to read method.

Semi colon means null, do nothing.

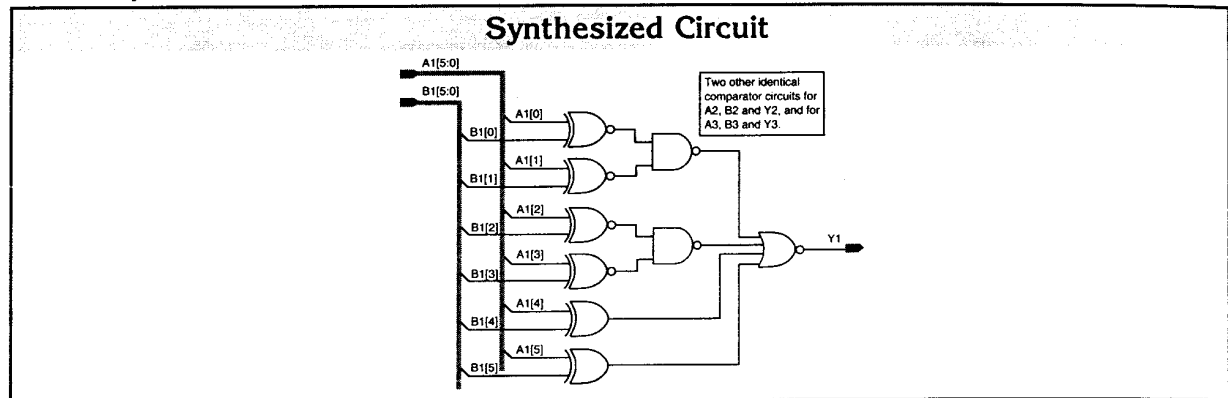
## Three ways to infer a 6-bit equality comparator



## Example 6.13 Multiple Comparison Comparator

Extra parentheses enclosing " $C \neq D$  or  $E \geq F$ " means that either one of these conditions and " $A = B$ " must be true for the output to be at logic 1.

## Comparator using multiple comparisons

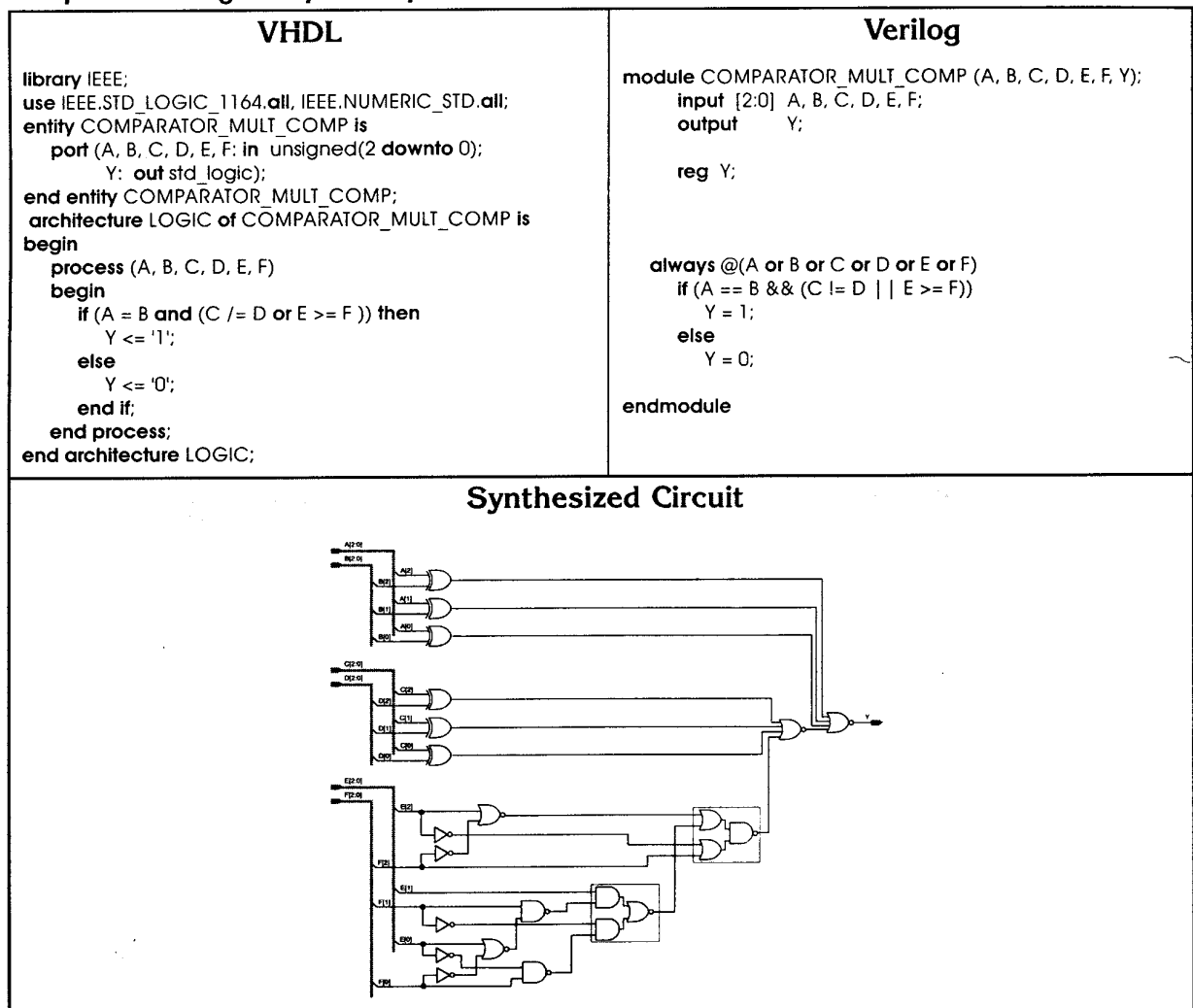

## ALU

An arithmetic logic unit (ALU) is the center core of a central processing unit (CPU). It consists of purely combinational logic circuit and performs a set of arithmetic and logic micro operations on two input busses. It has  $n$  encoded inputs for selecting which operation to perform. The select lines are decoded within the ALU to provide up to  $2^n$  different operations. The ALU in Example 6.14 is capable of performing 14 different micro operations.

### Example 6.14 An arithmetic logic unit

An Arithmetic Logic Unit (ALU) is modeled to the function table of Table 6.7.

| S4 | S3 | S2 | S1 | S0 | Cin | Operation                             | Function                   | Implementation block |
|----|----|----|----|----|-----|---------------------------------------|----------------------------|----------------------|
| 0  | 0  | 0  | 0  | 0  | 0   | $Y \leftarrow A$                      | Transfer A                 | Arithmetic Unit      |
| 0  | 0  | 0  | 0  | 0  | 1   | $Y \leftarrow A + 1$                  | Increment A                | Arithmetic Unit      |
| 0  | 0  | 0  | 0  | 1  | 0   | $Y \leftarrow A + B$                  | Addition                   | Arithmetic Unit      |
| 0  | 0  | 0  | 0  | 1  | 1   | $Y \leftarrow A + B + 1$              | Add with carry             | Arithmetic Unit      |
| 0  | 0  | 0  | 1  | 0  | 0   | $Y \leftarrow A + B_{\text{bar}}$     | A plus 1's complement of B | Arithmetic Unit      |
| 0  | 0  | 0  | 1  | 0  | 1   | $Y \leftarrow A + B_{\text{bar}} + 1$ | Subtraction                | Arithmetic Unit      |
| 0  | 0  | 0  | 1  | 1  | 0   | $Y \leftarrow A - 1$                  | Decrement A                | Arithmetic Unit      |
| 0  | 0  | 0  | 1  | 1  | 1   | $Y \leftarrow A$                      | Transfer A                 | Arithmetic Unit      |
| 0  | 0  | 1  | 0  | 0  | 0   | $Y \leftarrow A \text{ and } B$       | AND                        | Logic Unit           |
| 0  | 0  | 1  | 0  | 1  | 0   | $Y \leftarrow A \text{ or } B$        | OR                         | Logic Unit           |
| 0  | 0  | 1  | 1  | 0  | 0   | $Y \leftarrow A \text{ xor } B$       | XOR                        | Logic Unit           |
| 0  | 0  | 1  | 1  | 1  | 0   | $Y \leftarrow A_{\text{bar}}$         | Complement A               | Logic Unit           |
| 0  | 0  | 0  | 0  | 0  | 0   | $Y \leftarrow A$                      | Transfer A                 | Shifter Unit         |
| 0  | 1  | 0  | 0  | 0  | 0   | $Y \leftarrow \text{shl } A$          | Shift left A               | Shifter Unit         |
| 1  | 0  | 0  | 0  | 0  | 0   | $Y \leftarrow \text{shr } A$          | Shift right A              | Shifter Unit         |
| 1  | 1  | 0  | 0  | 0  | 0   | $Y \leftarrow 0$                      | Transfer 0's               | Shifter Unit         |

Table 6.7 ALU Function table

This whole function table could be modeled using a single **case** statement, however, its synthesized structure would be poor. Instead, the ALU has been modeled with a separate arithmetic unit, logic unit and shifter, as indicated by the modeled circuit structure. By separating the arithmetic and logic units in this way, and multiplexing their outputs to the shifter, better pre-optimized timing will result. It is very likely, that even after optimization, the shortest timing delay through the ALU will be longer if the arithmetic and logic units were combined into one process.

The arithmetic unit modeled using a single **case** statement. The reason it can be modeled in this way is because the synthesis tools from VeriBest Incorporated, synthesizes expressions like  $A + B + 1$  to a single adder with the carry in set to logic 1. If a synthesis tool is being used that does not support this, it is necessary to remodel it in a way that avoids multiple adders being synthesized. Provided the synthesis tools resource sharing option is turned on, the synthesized logic of the arithmetic unit will consist of just one adder for all add and subtract operations.

### Arithmetic logic unit

| VHDL  | Verilog   |
|---|---|
| <pre> library IEEE; use IEEE.STD_LOGIC_1164.all, IEEE.NUMERIC_STD.all; entity ALU is   port ( Sel:    in  unsigned(4 downto 0);         CarryIn: in  std_logic;         A, B:    in  unsigned(7 downto 0);         Y:       out unsigned(7 downto 0)); end entity ALU; </pre> | <pre> module ALU (Sel, CarryIn, A, B, Y);   input  (4:0) Sel;   input  CarryIn;   input  (7:0) A, B;   output (7:0) Y;   reg    (7:0) Y; </pre> |
| <i>continued</i>  | <i>continued</i>  |

## Arithmetic logic unit

| VHDL  | Verilog   |
|---|---|
| <pre> <b>architecture</b> COND_DATA_FLOW <b>of</b> ALU <b>is</b> <b>begin</b>   ALU_AND_SHIFT:     <b>process</b> (Sel, A, B, CarryIn)       <b>variable</b> Sel0_1_CarryIn: <b>unsigned</b>(2 <b>downto</b> 0);       <b>variable</b> LogicUnit, ArithUnit,         ALU_NoShift: <b>unsigned</b>(7 <b>downto</b> 0);     <b>begin</b>       -----       -- Logic Unit       -----       LOGIC_UNIT: <b>case</b> Sel(1 <b>downto</b> 0) <b>is</b>         <b>when</b> "00" =&gt; LogicUnit := A <b>and</b> B;         <b>when</b> "01" =&gt; LogicUnit := A <b>or</b> B;         <b>when</b> "10" =&gt; LogicUnit := A <b>xor</b> B;         <b>when</b> "11" =&gt; LogicUnit := <b>not</b> A;         <b>when others</b> =&gt; LogicUnit := (<b>others</b> =&gt; 'X');       <b>end case</b> LOGIC_UNIT;       -----       -- Arithmetic Unit       -----       Sel0_1_CarryIn := Sel(1 <b>downto</b> 0) &amp; CarryIn;       ARITH_UNIT: <b>case</b> Sel0_1_CarryIn <b>is</b>         <b>when</b> "000" =&gt; ArithUnit := A;         <b>when</b> "001" =&gt; ArithUnit := A + 1;         <b>when</b> "010" =&gt; ArithUnit := A + B;         <b>when</b> "011" =&gt; ArithUnit := A + B + 1;         <b>when</b> "100" =&gt; ArithUnit := A + <b>not</b> B;         <b>when</b> "101" =&gt; ArithUnit := A - B;         <b>when</b> "110" =&gt; ArithUnit := A - 1;         <b>when</b> "111" =&gt; ArithUnit := A;         <b>when others</b> =&gt; ArithUnit := (<b>others</b> =&gt; 'X');       <b>end case</b> ARITH_UNIT;       -----       -- Multiplex between Logic &amp; Arithmetic Units       -----       LA_MUX: <b>if</b> (Sel(2) = '1') <b>then</b>         ALU_NoShift := LogicUnit;       <b>else</b>         ALU_NoShift := ArithUnit;       <b>end if</b> LA_MUX;       -----       -- Shift operations       -----       SHIFT: <b>case</b> Sel(4 <b>downto</b> 3) <b>is</b>         <b>when</b> "00" =&gt; Y &lt;= ALU_NoShift;         <b>when</b> "01" =&gt; Y &lt;= Shift_left(ALU_NoShift, 1);         <b>when</b> "10" =&gt; Y &lt;= Shift_right(ALU_NoShift, 1);         <b>when</b> "11" =&gt; Y &lt;= (<b>others</b> =&gt; '0');         <b>when others</b> =&gt; Y &lt;= (<b>others</b> =&gt; 'X');       <b>end case</b> SHIFT;     <b>end process</b> ALU_AND_SHIFT; <b>end architecture</b> COND_DATA_FLOW; </pre> | <pre> <b>reg</b> (7:0) LogicUnit, ArithUnit,   ALU_NoShift;  <b>always</b> @(Sel <b>or</b> A <b>or</b> B <b>or</b> CarryIn) <b>begin</b>: ALU_PROC    -----   // Logic Unit   -----   <b>case</b> (Sel(1:0))     2'b 00 : LogicUnit = A &amp; B;     2'b 01 : LogicUnit = A   B;     2'b 10 : LogicUnit = A ^ B;     2'b 11 : LogicUnit = ! A;     <b>default</b> : LogicUnit = 8'b X;   <b>endcase</b>   -----   // Arithmetic Unit   -----   <b>case</b> ((Sel(1:0), CarryIn))     3'b 000 : ArithUnit = A;     3'b 001 : ArithUnit = A + 1;     3'b 010 : ArithUnit = A + B;     3'b 011 : ArithUnit = A + B + 1;     3'b 100 : ArithUnit = A + ! B;     3'b 101 : ArithUnit = A - B;     3'b 110 : ArithUnit = A - 1;     3'b 111 : ArithUnit = A;     <b>default</b> : ArithUnit = 8'b X;   <b>endcase</b>   -----   // Multiplex between Logic &amp; Arithmetic Units   -----   <b>if</b> (Sel(2))     ALU_NoShift = LogicUnit;   <b>else</b>     ALU_NoShift = ArithUnit;   -----   // Shift operations   -----   <b>case</b> (Sel(4:3))     2'b 00 : Y = ALU_NoShift;     2'b 01 : Y = ALU_NoShift &lt;&lt; 1;     2'b 10 : Y = ALU_NoShift &gt;&gt; 1;     2'b 11 : Y = 8'b 0;     <b>default</b> : Y = 8'b X;   <b>endcase</b> <b>end</b> <b>endmodule</b> </pre> |

Separate VHDL concatenation. Cannot be incorporated in case expression like Verilog.

## Modeled Circuit Structure

